

NOVEDAD

$$\vec{v}_A = \frac{q}{m} \vec{E} = \mu \vec{E}$$

$$I(t) = \frac{dq}{dt} = m q A v_A \quad [I] = \frac{C}{s} = A \quad [\vec{j}] = \frac{A}{m^2}$$

$$I = \int_A \vec{j} \cdot d\vec{s} \quad \text{si } \vec{j} \perp d\vec{s} \Rightarrow \oint \vec{j} \cdot d\vec{s} = 0 \vee \vec{\nabla} \cdot \vec{j} = 0 \quad \left\{ \begin{array}{l} I \parallel \vec{j} \Rightarrow |\vec{j}| = \frac{I}{A} \Rightarrow \vec{j} = \frac{m q^2}{2} \vec{E} \\ \sigma_1 < \sigma_2 \Rightarrow m_{01} > m_{02} \end{array} \right. \quad \sigma = m_0^{-1}$$

$\uparrow T \Rightarrow \downarrow G \Rightarrow \downarrow v_A \Rightarrow \downarrow I \Rightarrow \downarrow \sigma \Rightarrow \uparrow B$

$(\uparrow L \Rightarrow \uparrow R), (\downarrow A \Rightarrow \uparrow R) \quad R = \frac{m I}{A} = \frac{1}{A \tau} \quad \Delta V = R I \quad [R] = \Omega \quad [P] = \frac{J}{s} = W (Watts)$

$V_{PILA} = \mathcal{E} = \frac{C \Delta V^2}{2} = \frac{Q^2}{2C}$, $V_{capacitor} = \mathcal{E}_C$, $V_{RESISTENCIA} = I R$

LEY DE LOS NODOS $\rightarrow \sum_{i=1}^n I_i = 0$ (CON SIGNOS)
 LEY DE LAS MALLAS $\rightarrow \sum \Delta V = 0$ (CON SIGNOS)

$\{ \exists \{ R_1, \dots, R_m \} / R_1 \Sigma R_2 \Sigma \dots \Sigma R_m \Rightarrow R_{eq} = \sum_{i=1}^m R_i$
 $\{ \exists \{ R_1, \dots, R_m \} / R_1 // R_2 // \dots // R_m \Rightarrow R_{eq}^{-1} = \sum_{i=1}^m R_i^{-1}$

$P_{PILA} = I V_{PILA}$
 $P_{RESISTENCIA} = \frac{\Delta V_{RESISTENCIA}^2}{R}$

$P_{ENTREGADA} = P_{DISIPADA} + P_{ABSORBIDA} \Leftrightarrow$ solo con el circuito completo

$\hookrightarrow \sum_{k=1}^n I_k \mathcal{E}_k = \sum_{i=1}^n I_i^2 R_i + \sum_{j=1}^r I_j \mathcal{E}_j \quad \left\{ \begin{array}{l} V_{terminal} = 0 \Rightarrow I_{terminal} = 0 \\ ENTREGA \\ ABSORBE \end{array} \right.$

$I_A \Sigma I_B \Rightarrow I_A = I_B \quad E [kWh] = POTENCIA [kW] \times HORAS / 1000$

$\oint \vec{B} \cdot d\vec{s} = 0 \Rightarrow \vec{\nabla} \cdot \vec{B} = 0 \quad \vec{F}_{m \text{ sobre } q} = q(\vec{v} \times \vec{B}) / W_{Fm} = 0 \wedge \vec{F}_{m} \parallel \vec{v}$

$\vec{F}_L = q \vec{E} + q(\vec{v} \times \vec{B})$ Trayectoria helicoidal (MCU + MRU) $\vec{B} = B_0 \hat{j}, \vec{v} = v_x \hat{i} + v_z \hat{j}$

$\vec{F}_m = I \oint_P d\vec{l} \times \vec{B} = I |\vec{r}_p - \vec{r}_q| B_0 \hat{m} \Leftrightarrow \vec{B}$ UNIFORME

$K_{magnetic} = \frac{\mu_0}{4\pi r} \Rightarrow \vec{B}(r) = \frac{\mu_0 q}{4\pi} \frac{\vec{v} \times (\vec{r} - \vec{r}')}{|\vec{r} - \vec{r}'|^3}$

$\vec{B}(r) = \begin{cases} K_m \int I \frac{d\vec{l} \times (\vec{r} - \vec{r}')}{|\vec{r} - \vec{r}'|^3} \leftarrow 1D \\ K_m \iint \vec{k} \frac{d\vec{s} \times (\vec{r} - \vec{r}')}{|\vec{r} - \vec{r}'|^3} \leftarrow 2D \\ K_m \iiint \vec{j} \frac{d\vec{v} \times (\vec{r} - \vec{r}')}{|\vec{r} - \vec{r}'|^3} \leftarrow 3D \end{cases}$

Ley de Ampere $\rightarrow \oint \vec{B}(r) \cdot d\vec{l} = \mu_0 I_{enc}$

Ley de Ampere Generalizada L.H. $\left\{ \begin{array}{l} \vec{B} = \mu_0 (\vec{H} + \vec{M}) \\ \vec{M} = \chi_m \vec{H} = \mu_0 \chi_m \vec{H} \end{array} \right. \quad \begin{array}{l} I \parallel \vec{m} \Rightarrow +I \\ I \nparallel \vec{m} \Rightarrow -I \end{array}$

Ley de Ampere (para corrientes estacionarias) $\rightarrow \oint_C \vec{B} \cdot d\vec{l} = \mu_0 \{ \sum I_s(a) \}$

$\vec{B}(r) |_{r \rightarrow \infty} = \frac{\mu_0 I}{2\pi r} \hat{\phi}$

$m: \text{'DEMOSTRACION DE ESPINAS'} = \frac{N}{L} \Rightarrow I N = I_{enc} = \vec{B}_s(r) = \int \dots \int \vec{B}(r') \cdot d\vec{l} N \quad \left\{ \begin{array}{l} \vec{\nabla} \times \vec{E} = -\frac{d\vec{B}}{dt} \end{array} \right.$

$[B] = T (E.S.I.) \quad [H] = [M] = A/m \quad \mu = \mu_r \mu_0 \wedge \mu_r |_{vacuo} = 1$

TORONDE $\left\{ \begin{array}{l} \vec{B} = \frac{\mu_0 \mu_r N I}{2\pi r} \\ L = \frac{\mu_0 \mu_r N^2 S}{2\pi r} \end{array} \right.$

SOLENOIDE $\left\{ \begin{array}{l} \vec{B} = \mu_0 \mu_r N I \hat{z} / h \\ L = \mu_0 \mu_r N^2 S / h \\ M = \mu_0 \mu_r N_1 N_2 S_{12} / l \end{array} \right.$

OLIMPO MUELLO $\left\{ \begin{array}{l} \mu_0 I_1 r \hat{\phi} / 2 \leftarrow r < R_a \\ \mu_0 I_1 R_a^2 \hat{\phi} / 2r \leftarrow R_a < r < R_b \\ \mu_0 [I_1 R_a^2 + I_2 (r^2 - R_b^2)] \hat{\phi} / 2r \\ \mu_0 [I_1 R_a^2 + I_2 (R_c^2 - R_b^2)] \hat{\phi} / 2r \end{array} \right.$

$\oint \vec{B}(r) \cdot d\vec{l} = \mu_0 (I_r + I_m) = \mu_0 (\oint \vec{H}(r) \cdot d\vec{l} + \oint \vec{M}(r) \cdot d\vec{l}) = \mu_0 (\vec{H} + \vec{M})$

$\mathcal{E}_{FEM} = -\frac{d\phi}{dt} = -\frac{d}{dt} \int \vec{B} \cdot d\vec{s} = \lambda_{ind} \cdot R$

$\frac{d\phi}{dt} > 0 \Rightarrow \frac{dI}{dt} > 0 \Rightarrow \mathcal{E} < 0 \Rightarrow \text{SIGN}(i_{ind}) = -\text{SIGN}(i)$

$\mathcal{E} < 0 \Rightarrow I_{ind} < 0 \Rightarrow$ LA CORRIENTE INDUCIDA VA EN LA DIRECCION CONTRARIA QUE LA ORIGINAL

$\frac{d\phi}{dt} < 0 \Rightarrow \frac{dI}{dt} < 0 \Rightarrow \mathcal{E} > 0 \Rightarrow \text{SIGN}(i_{ind}) = \text{SIGN}(i)$

NOTA $\{ \tan(\varphi_i) = R(\omega C - \frac{1}{\omega L}) \}$

$$\left\{ \begin{array}{l} \bar{B} \in \text{ENTRANTE} \wedge \left| \frac{dB}{dt} \right| > 0 \Rightarrow \bar{E} \in \text{SALIENTE} \\ \bar{B} \in \text{ENTRANTE} \wedge \left| \frac{dB}{dt} \right| < 0 \Rightarrow \bar{E} \in \text{ENTRANTE} \end{array} \right.$$

$$\left\{ \begin{array}{l} \bar{B} \in \text{SALIENTE} \wedge \left| \frac{dB}{dt} \right| > 0 \Rightarrow \text{ENTRANTE} \\ \bar{B} \in \text{SALIENTE} \wedge \left| \frac{dB}{dt} \right| < 0 \Rightarrow \text{SALIENTE} \end{array} \right.$$

$$M = M_1 Z = M_2 Z$$

$$E_{\text{total}} = N \cdot E_{\text{inducida}}$$

$$\left\{ \begin{array}{l} \varepsilon_{11} = -\frac{N_1 \phi_{11}}{dt} = -\frac{N_1 \phi_{11}}{dt} \cdot \frac{di_1}{dt} = -L \frac{di_1}{dt} \\ \varepsilon_{22} = -\frac{N_2 \phi_{22}}{dt} = -\frac{N_2 \phi_{22}}{dt} \cdot \frac{di_2}{dt} = -M \frac{di_2}{dt} \end{array} \right.$$

$$U = \frac{LI^2}{2}$$

$$\frac{df}{dt} \approx \frac{\Delta f}{\Delta t} = \frac{f(t_1) - f(t_0)}{t_1 - t_0} \Leftrightarrow \exists t_0, t_1, f(t_0), f(t_1)$$

$$[m] = N/L$$

BOBINES
HOMÓLOGAS

$$\left\{ \begin{array}{l} \varepsilon = -(L_1 + L_2 + 2M) \frac{di}{dt} \\ \varepsilon_1 = -L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} \\ \varepsilon_2 = -L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} \end{array} \right.$$

BOBINES
HOMÓLOGAS

$$\left\{ \begin{array}{l} \varepsilon = -(L_1 + L_2 - 2M) \frac{di}{dt} \\ \varepsilon_1 = -L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} \\ \varepsilon_2 = -L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} \end{array} \right.$$


$$c/p = \cos \phi_{LA}$$

$$s/p = \sin \phi_{LA}$$

$$V_{\text{INDUCIDA}} = L \frac{di}{dt}$$


RL
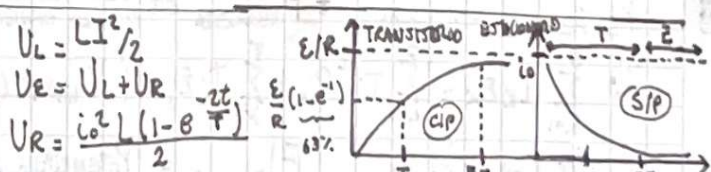
$$\left\{ \begin{array}{l} i(0) = 0, i(t) = \frac{\varepsilon}{R} (1 - e^{-\frac{R}{L}t}), T = \frac{L}{R}, U_L = LI^2/2 \\ i(0) = i_0, i(t) = i_0 e^{-\frac{R}{L}t}, U_R = \frac{i_0^2 L (1 - e^{-\frac{R}{L}t})}{2} \end{array} \right.$$




LC
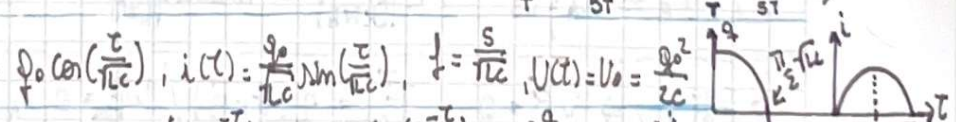
$$\left\{ \begin{array}{l} q(0) = q_0, i(0) = 0, q(t) = q_0 \cos(\frac{t}{\sqrt{LC}}), i(t) = \frac{q_0}{\sqrt{LC}} \sin(\frac{t}{\sqrt{LC}}), \frac{1}{T} = \frac{1}{\sqrt{LC}}, U(t) = U_0 = \frac{q_0^2}{2C} \end{array} \right.$$




RC
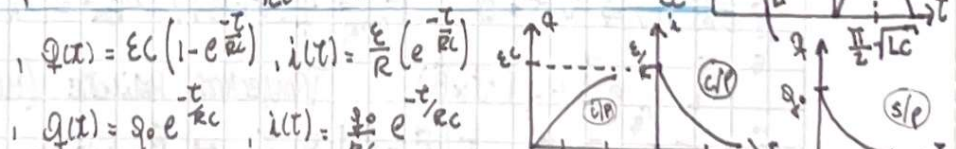
$$\left\{ \begin{array}{l} T = RC \\ U_E(t) \xrightarrow{CE^2} CE^2 \\ U_R(t), U_C(t) \xrightarrow{CE^2} CE^2 \end{array} \right.$$



RLC
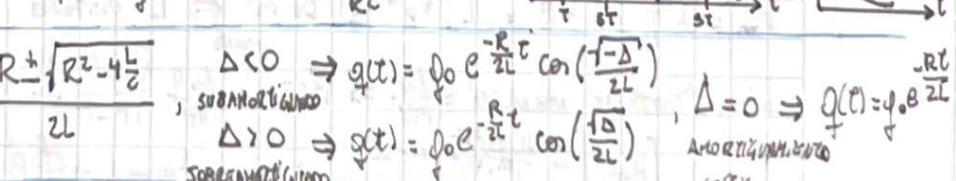
$$\left\{ \begin{array}{l} q(0) = q_0, q(t) = A e^{\lambda t} \\ i(0) = 0, i(t) = A \lambda e^{\lambda t} \end{array} \right. \quad \lambda = \frac{-R \pm \sqrt{R^2 - 4L}}{2L}$$



RESISTIVO PURO

$$\left\{ \begin{array}{l} i(t) = \frac{V_0}{R} \cos(\omega t + \phi_v) \\ i_0 = \frac{V_0}{R}, \phi_i = \phi_v, \phi_{ir} = 0 \end{array} \right.$$

CAPACITIVO PURO

$$\left\{ \begin{array}{l} q(t) = C V_0 \cos(\omega t + \phi_v) \\ i_0 = C \omega V_0, \phi_{ir} = \pi/2, \phi_{ic} = (\omega C)^{-1} \end{array} \right.$$

INDUCTIVO PURO

$$\left\{ \begin{array}{l} i(t) = \frac{V_0}{\omega L} \cos(\omega t + \phi_v - \frac{\pi}{2}) \\ i_0 = \frac{V_0}{\omega L}, \phi_{ir} = -\frac{\pi}{2}, \phi_{il} = \omega L \end{array} \right.$$

PSEUDO Ley de OHM $\rightarrow V_p = IZ \rightarrow V_0 e^{j\phi_v} = i_0 e^{j\phi_i} Z \Rightarrow \left\{ \begin{array}{l} V_0 = i_0 |Z| \\ \phi_v = \phi_i + \phi_Z \Rightarrow \phi_Z = -\phi_{ir} \end{array} \right.$

$Z = Z_R + Z_L + Z_C = R + j\omega L + (-j\frac{1}{\omega C})$, $V_{EF} = \frac{V_0}{\sqrt{2}}$, $i_{EF} = \frac{i_0}{\sqrt{2}}$, $[P] = W$, $[Q] = VAR$, $[S] = VA$

FACTORES DE POTENCIA

$$\left\{ \begin{array}{l} P = V_{EF} i_{EF} \cos(\phi_Z) = i_{EF}^2 R, \phi_Z = \pm \frac{\pi}{2} \Rightarrow P = 0 \\ Q = V_{EF} i_{EF} \sin(\phi_Z) = i_{EF}^2 (X_L - X_C), \phi_Z = 0 \Rightarrow Q = 0 \\ S = \sqrt{P^2 + Q^2} = V_{EF} i_{EF} \end{array} \right.$$

CIRCUITO EN RESONANCIA

$$\left\{ \begin{array}{l} \omega_r = (LC)^{-1/2} \\ i_{MAX} = V_0/R \\ P = V_{EF}^2/R \end{array} \right.$$

W_{LZ} = $\pm \frac{CR + \sqrt{C^2 R^2 + 4LC}}{2LC}$

(EN RESONANCIA)

$$\left\{ \begin{array}{l} X_L = \omega L, X_C = \frac{1}{\omega C} \end{array} \right.$$

FACTORES DE POTENCIA: $\cos(\phi_Z)$ FRECUENCIAS DE P = $\frac{P_{MAX}}{2}$

CAPACITIVO $\left\{ \begin{array}{l} X_L < X_C, Q < 0 \\ \phi_Z < 0, \phi_{ir} > 0 \end{array} \right.$ INDUCTIVO $\left\{ \begin{array}{l} X_L > X_C, Q > 0 \\ \phi_Z > 0, \phi_{ir} < 0 \end{array} \right.$

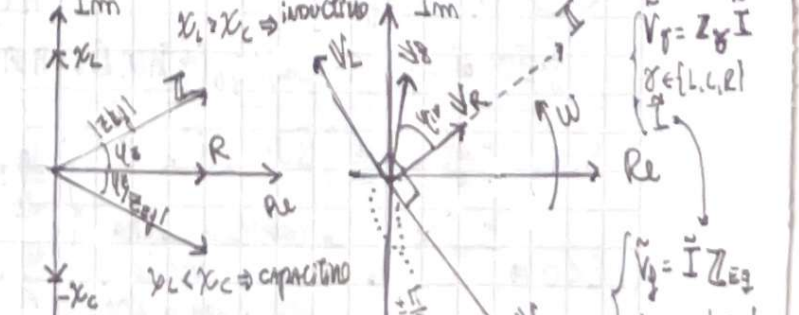


DIAGRAMA DE IMPEDANCIAS $\{ I(t) = |I| \cos(\omega t + \phi_i) / |I| = |V_g| / |Z| \}$